

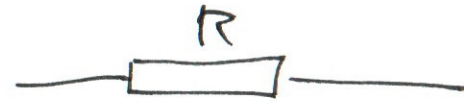


Electrical Networks

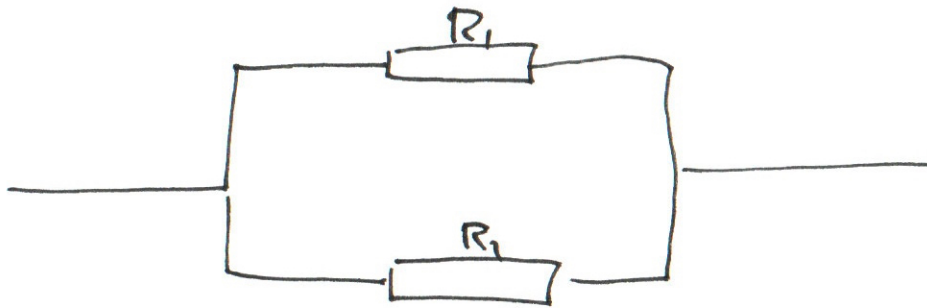

$\equiv$

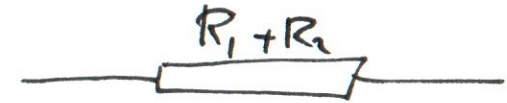

$\equiv$

$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


A circuit diagram showing a single equivalent resistor, representing the parallel combination of R_1 and R_2 .

Ohm's Law $R = \frac{V}{I}$

V = potential difference or voltage


I = current.

II

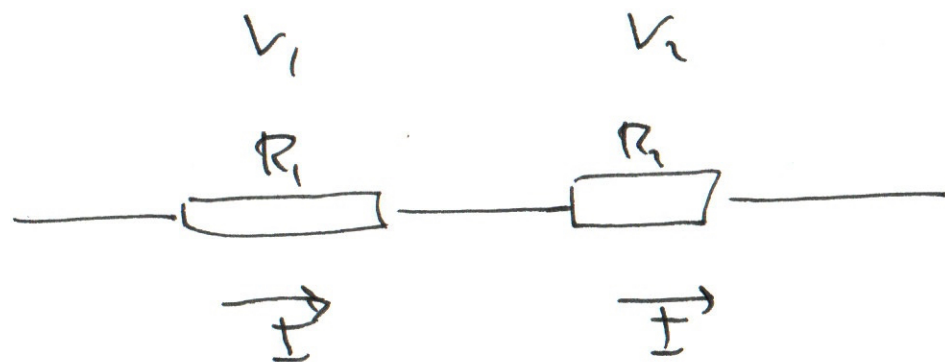

$$V = V_1 + V_2$$
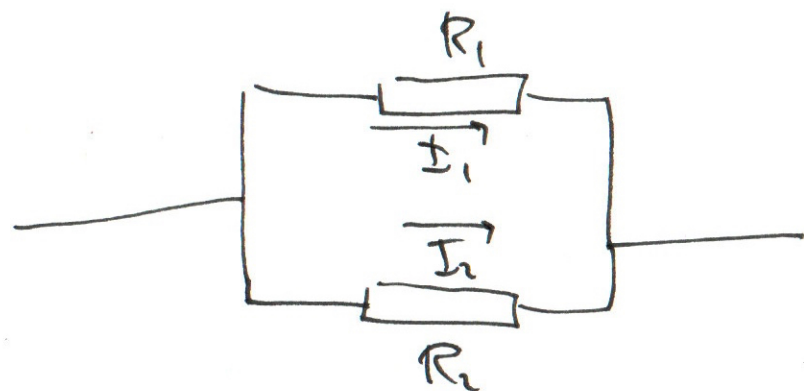
$$R = \frac{V}{I} = \frac{V_1 + V_2}{I} = \frac{V_1}{I} + \frac{V_2}{I} = R_1 + R_2$$






$$\frac{1}{R} = \frac{I}{V} = \frac{I_1 + I_2}{V} =$$


$$= \frac{I_1}{V} + \frac{I_2}{V} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

III

Each edge is
a unit resistor.

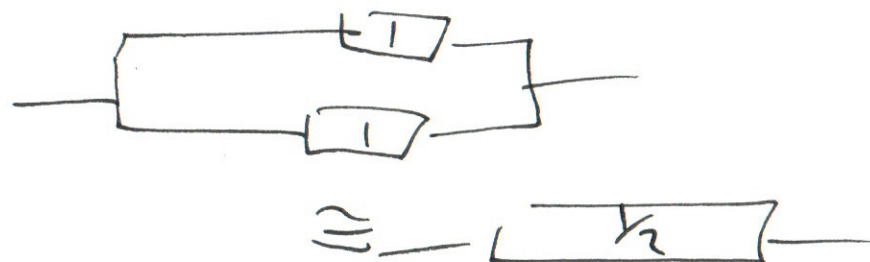
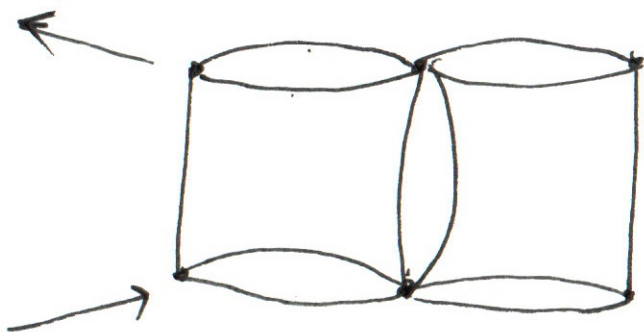
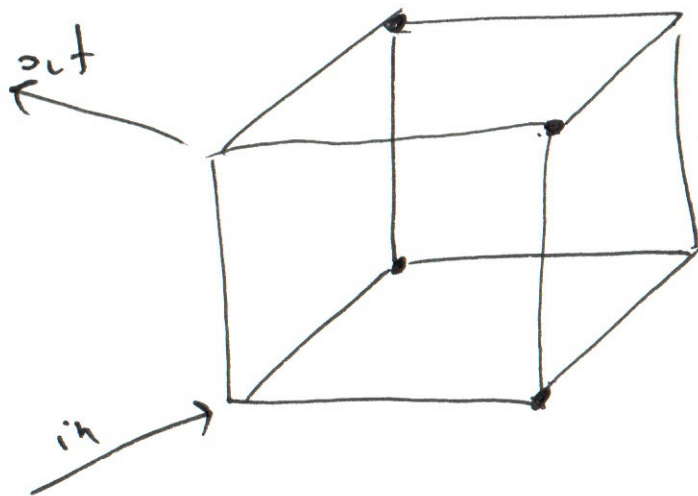


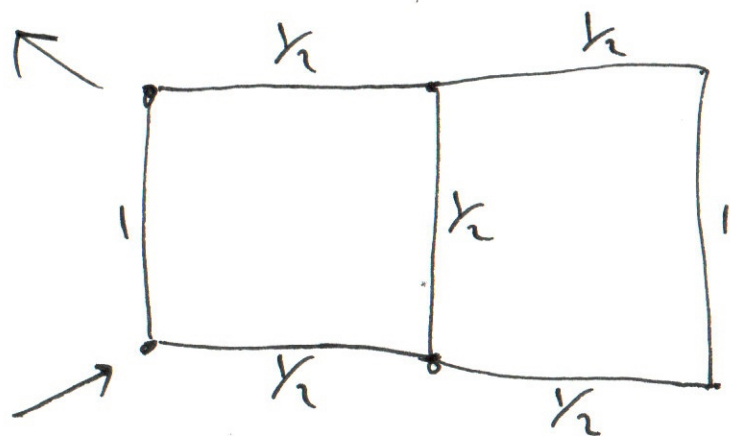

$$\frac{1}{\frac{1}{2} + \frac{1}{2}} =$$

$$\frac{1}{2 + \frac{1}{2}} = \frac{1}{\frac{5}{2}} = \frac{2}{5}$$

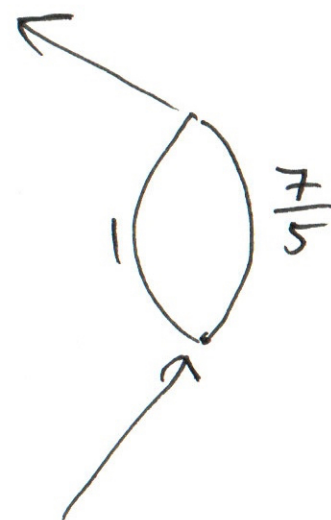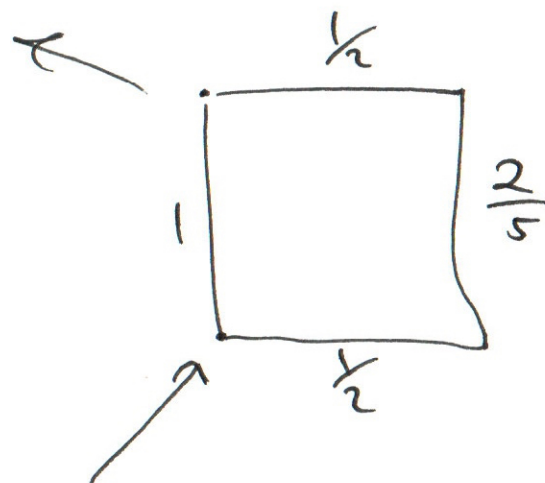
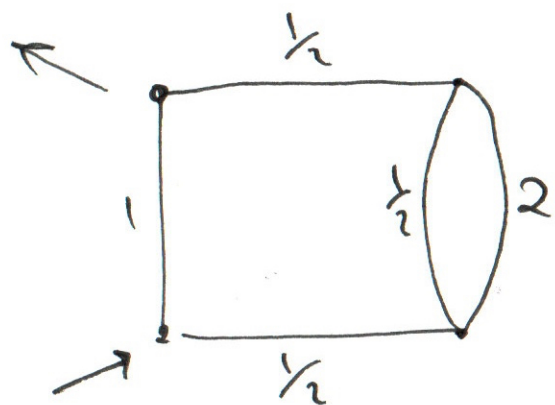
$$\frac{1}{2} + \frac{2}{5} + \frac{1}{2} = \frac{7}{5}$$



IV

$$\frac{1}{1 + \frac{1}{7/5}} =$$
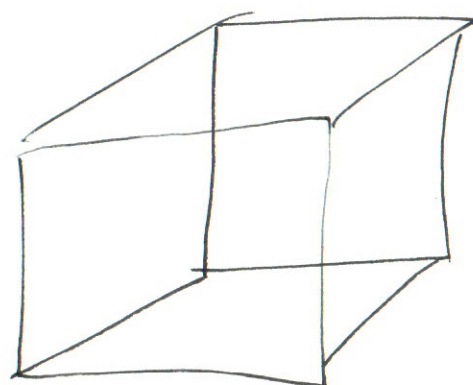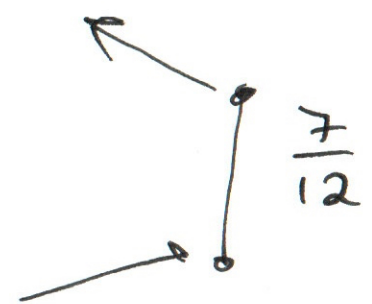
$$\frac{1}{1 + \frac{5}{7}} = \frac{1}{\frac{12}{7}} = \frac{7}{12}$$






$$f_1 = 12$$

$$f_0 - 1 = 7 = \text{\# edges in a spanning tree}$$

Then Let G be a graph and xy an edge □
 in the graph. Replace each edge with a unit resistor.
 Then the total resistance between nodes x and y
 is given by

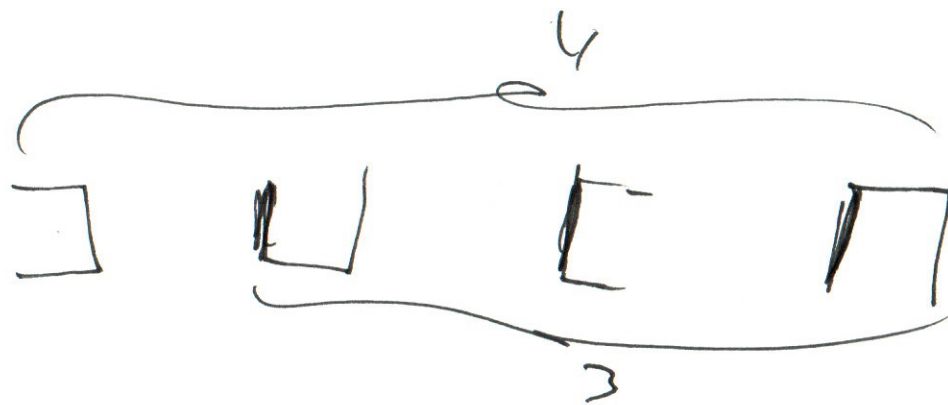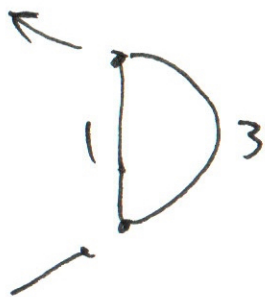
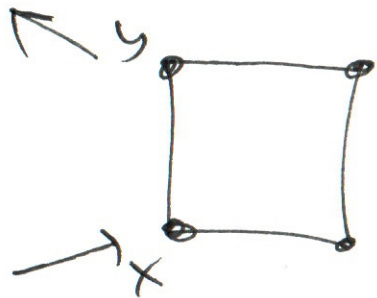
$$\frac{\# \text{ spanning trees in } T \text{ containing the edge } xy}{\# \text{ spanning trees.}}$$



VII

$$\frac{3}{4}$$
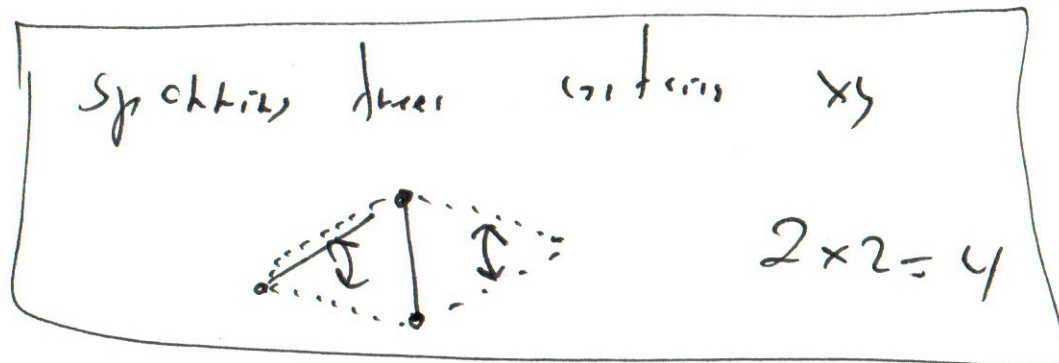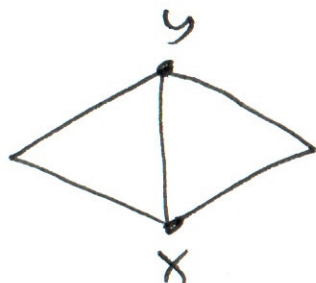
$$\frac{1}{\frac{1}{1} + \frac{1}{3}} = \frac{1}{\frac{4}{3}} = \frac{3}{4}$$




$$R_{xy} = \frac{4}{8} = \frac{1}{2}$$




4

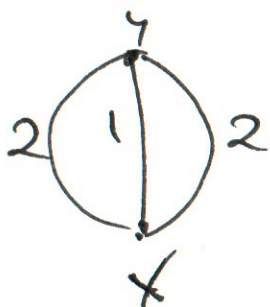
$$\# \text{ spektrale Dimensionen} = 4 + 4 = 8$$


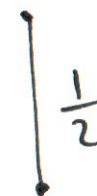
$$\frac{1}{\frac{1}{2} + 1 + \frac{1}{2}} = \frac{1}{2}$$



IX

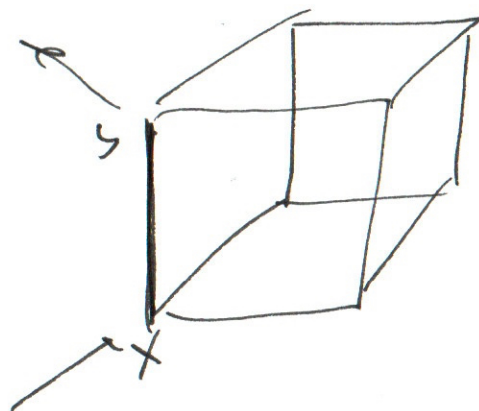

spectral lines = bss number.

$N = \# \text{ spectral lines}$

$N_e = \# \text{ spectral lines containing a given edge}$

Count pairs (T, e) where T is
a spanning tree, e ~~is~~ an edge and $e \notin T$.

8

$$\begin{array}{ccccc}
 N & \cdot & 7 & = & 12 \cdot N_e \\
 \uparrow & & \uparrow & & \uparrow \\
 \text{pick tree} & & \text{pick the} & & \text{pick the} \\
 & & \text{edge} & & \text{edge}
 \end{array}$$

$$\frac{7}{12} = \frac{N_e}{N} = \text{total resistance between } x \text{ and } y.$$


I (→ schedule)

Resistant to x_3 (x_3 is a c.d.)


$$= \frac{f_0 - 1}{f_1} = \frac{12 - 1}{30} = \frac{11}{30}$$

XII

IL first grid

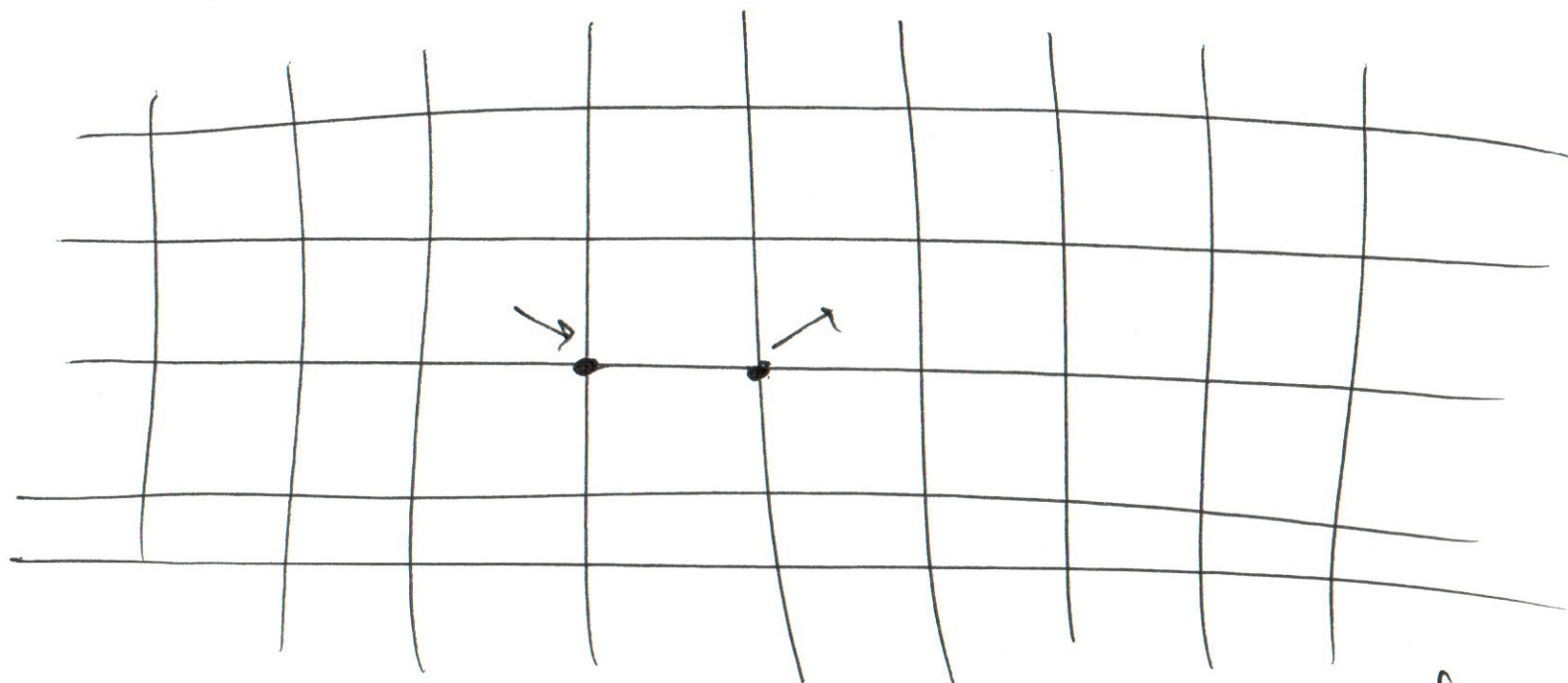

$\frac{1}{2}$

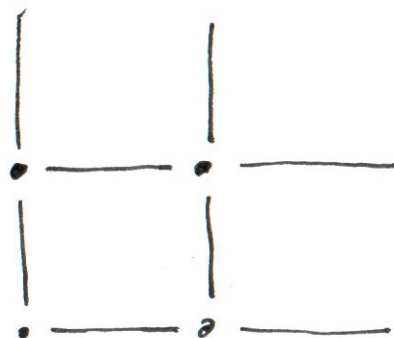


$$\frac{f_0 - 1}{f_1}$$


$$2. f_0 = f_1$$

$$\frac{f_0}{f_1} = \left(\frac{1}{2} \right)$$

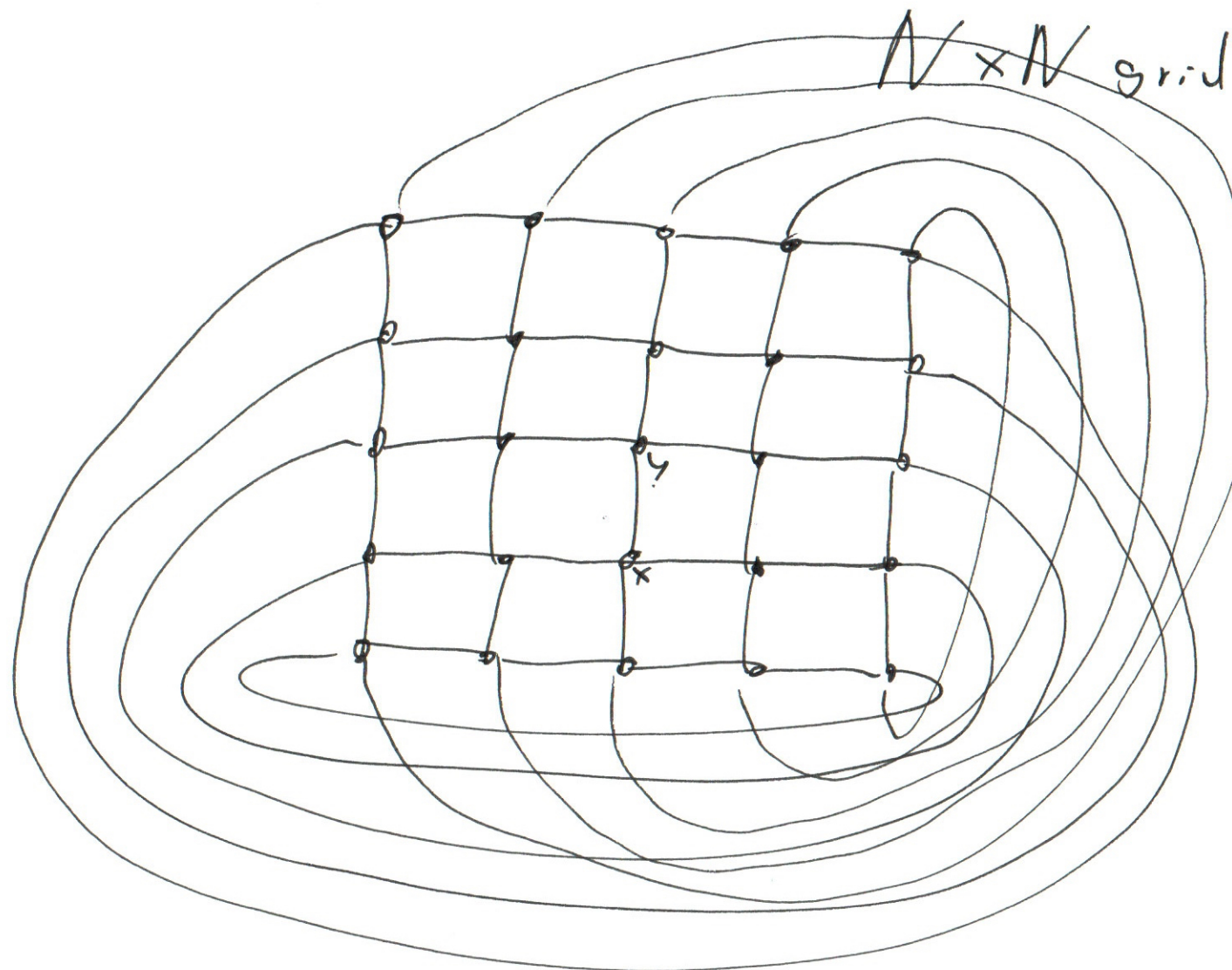Bul
 $f_0 - 1 \approx f_0$
 since
 $f_0 \rightarrow \infty$



Torus

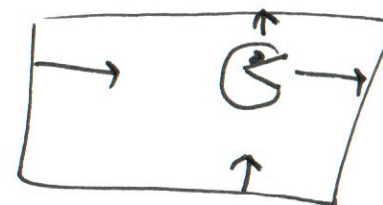


$$f_0 = N^2$$

$$f_1 = 2N^2$$

$$R_{xy} = \frac{f_0 - 1}{f_1} = \frac{N^2 - 1}{2N^2} \xrightarrow{N \rightarrow +\infty} \frac{1}{2}$$

XIV

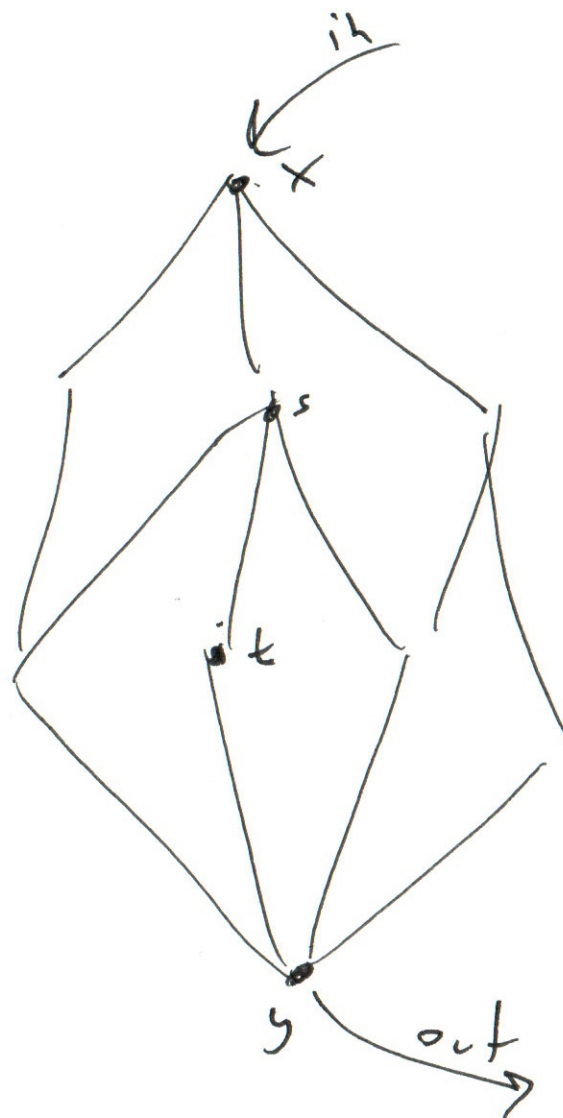

Each edge is
a unit resistor.

$$I_{st} = V_{st} = \overbrace{\quad}^{\text{Then...}}$$

$$= \frac{N(x, s, t, y) - N(x, t, s, y)}{N}$$

$N =$ total number of deer

$$N(x, s, t, y) =$$



$$N(x, t, s, y) =$$

